
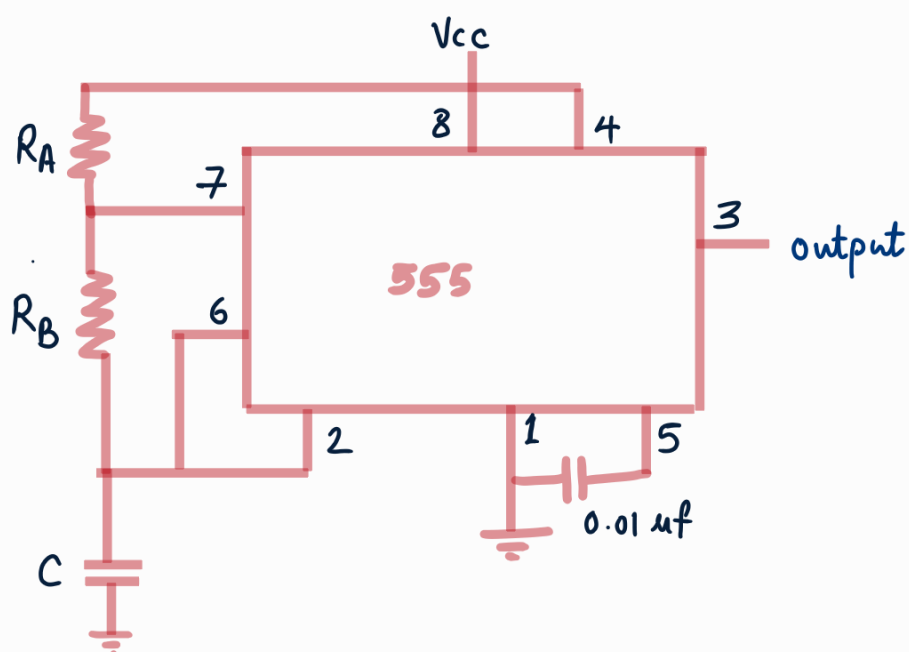


555 timer as an Astable Multivibrator


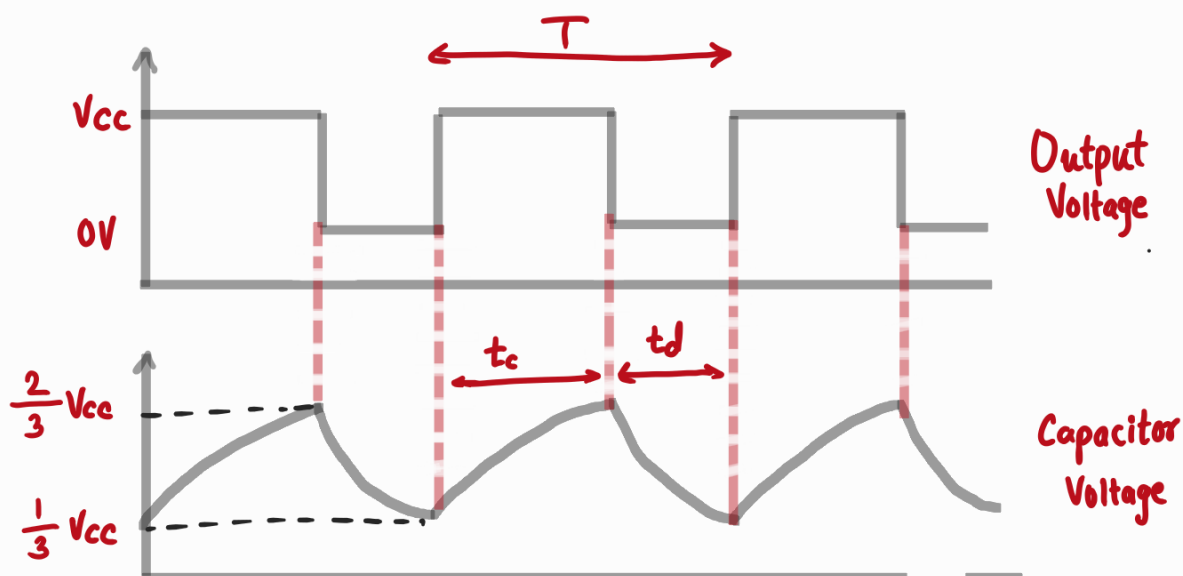
- free running
- Does not require external trigger



Circuit Diagram



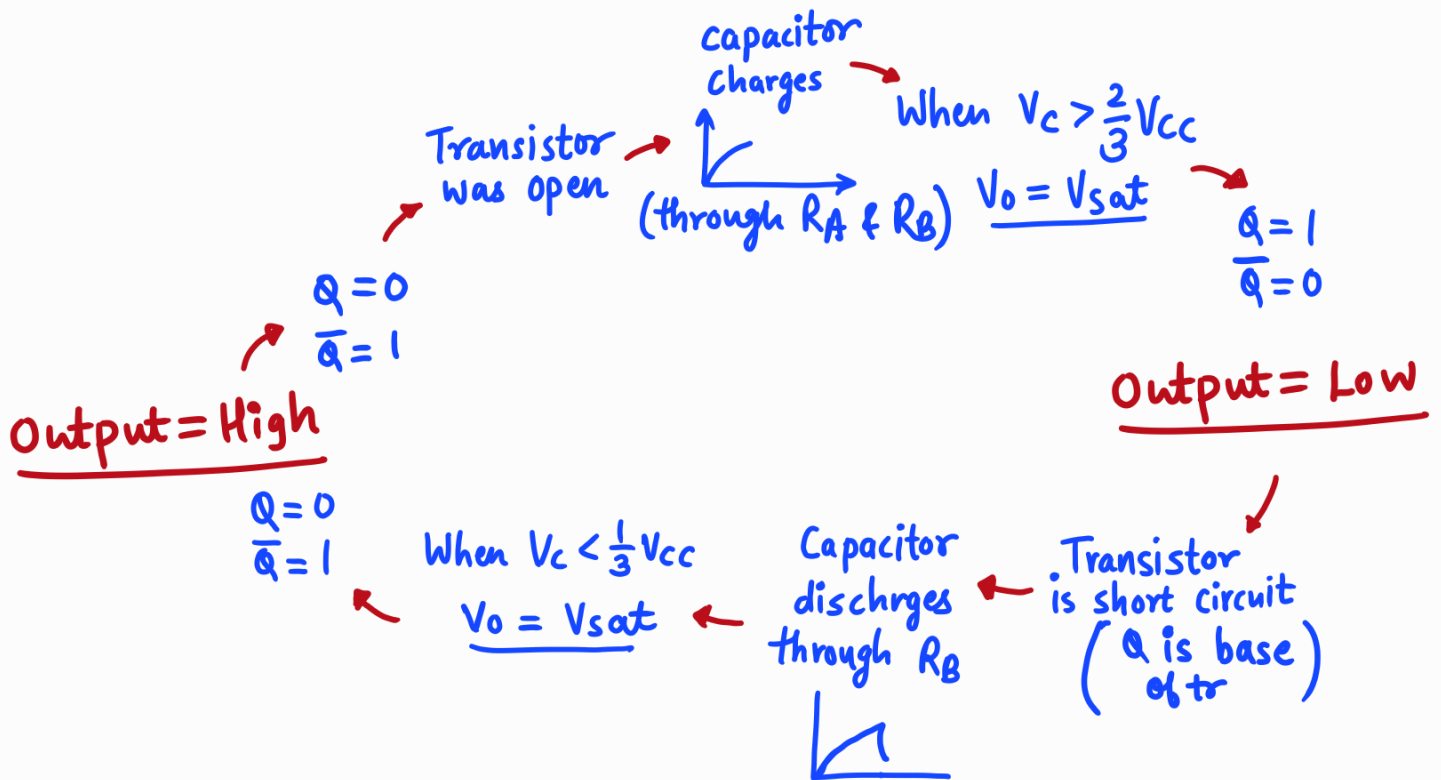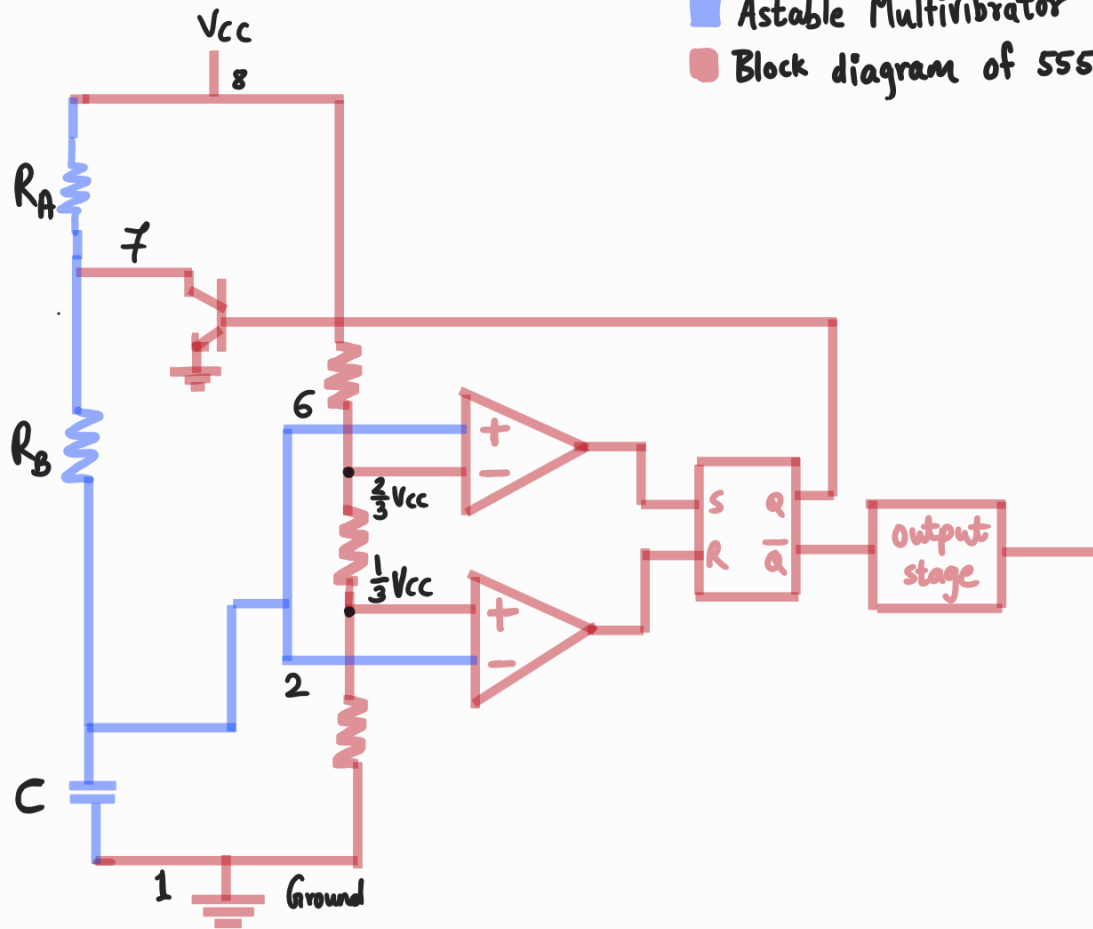- Astable Multivibrator
- Block diagram of 555



Initially output = High

C starts charging toward V_{CC}
through R_A and R_B

When $V_C = \frac{2}{3} V_{CC}$

Comparator 1 output = High

Flip flop sets ($S=1$)

$Q = 1$ $\bar{Q} = 0$

Output = $\bar{Q} = 0$ (Low)

Capacitor C starts discharging
through R_B and transistor

When $V_C = \frac{1}{3} V_{CC}$

Comparator 2 o/p = 1

FF resets $Q = 0$ $\bar{Q} = 1$

Output = 1 (High)

$$\text{charging time} = t_c = 0.69(R_A + R_B)C$$

$$\text{Discharging time} = t_d = 0.69(R_B)C$$

$$T = t_c + t_d = 0.69(R_A + 2R_B)C$$

$$\text{frequency of oscillations} = f_o = \frac{1}{T} = \frac{1.45}{(R_A + 2R_B)C}$$

$$\text{Duty cycle} = \frac{t_c}{T} \times 100$$

$$= \frac{R_A + R_B}{R_A + 2R_B} (100)$$

