

# Logic Gates

Md. Rokanujjaman  
Professor  
Dept. of CSE, RU

# Introduction

- Digital systems are concerned with digital signals
- Digital signals can take many forms
- Here we will concentrate on **binary signals** since these are the most common form of digital signals
  - can be used individually
    - perhaps to represent a single binary quantity or the state of a single switch
  - can be used in combination
    - to represent more complex quantities

# Boolean Constants and Variables


- Boolean 0 and 1 do not represent actual numbers but instead represent the state, or logic level.

Logic 0	Logic 1
False	True
Off	On
Low	High
No	Yes
Open switch	Closed switch

# Truth Tables


- A truth table is a means for describing how a logic circuit's output depends on the logic levels present at the circuit's inputs.

Inputs		Output
A	B	x
0	0	1
0	1	0
1	0	1
1	1	0

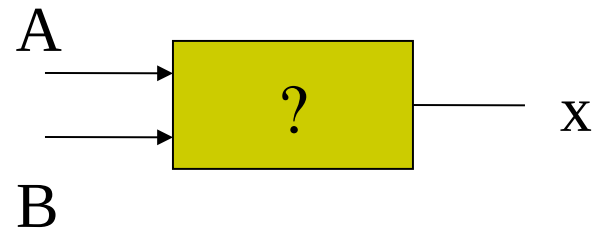
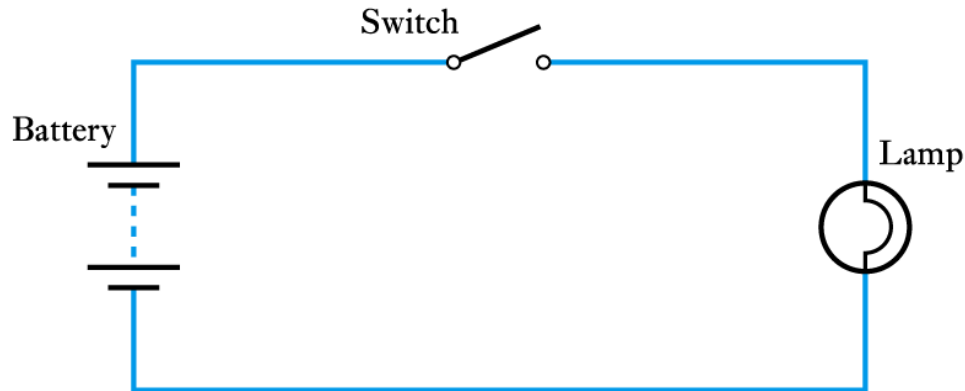
# Binary Quantities and Variables

- A **binary quantity** is one that can take only 2 states



A simple binary arrangement


<i>S</i>	<i>L</i>
OPEN	OFF
CLOSED	ON

<i>S</i>	<i>L</i>
0	0
1	1

A truth table

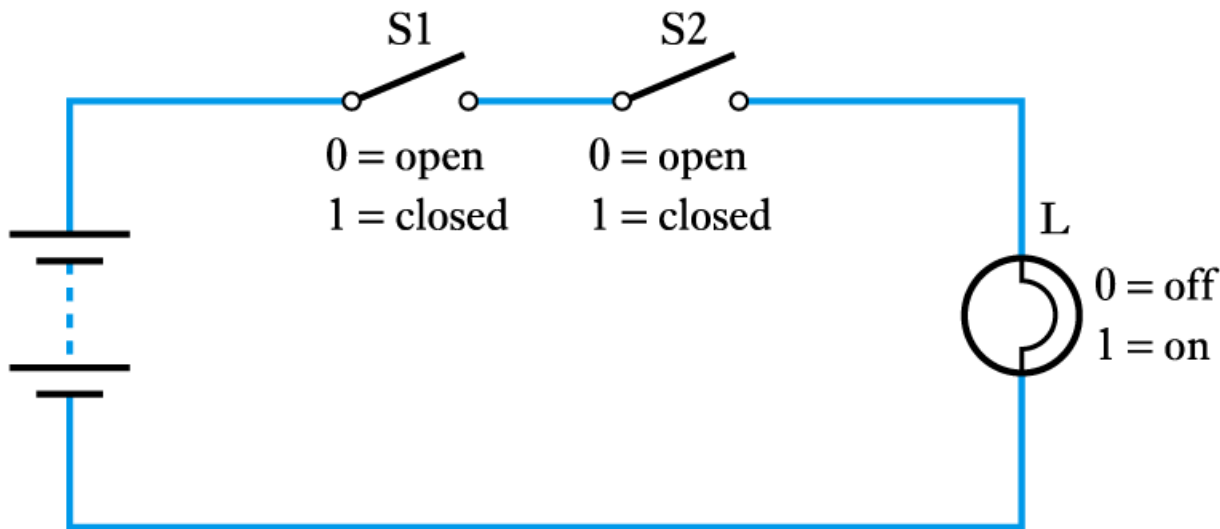- A binary arrangement with two switches in series




(a) Circuit

S1	S2	L
0	0	0
0	1	0
1	0	0
1	1	1

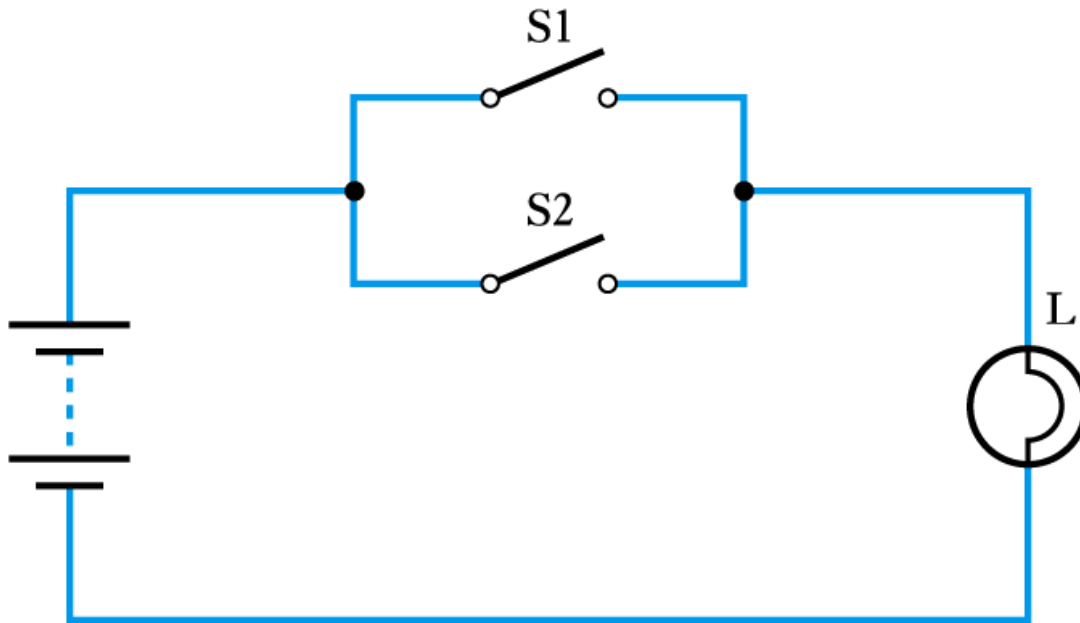(b) Truth table

$$L = S1 \text{ AND } S2$$

- A binary arrangement with two switches in parallel




(a) Circuit

S1	S2	L
0	0	0
0	1	1
1	0	1
1	1	1

(b) Truth table

$$L = S1 \text{ OR } S2$$

- Three switches in series

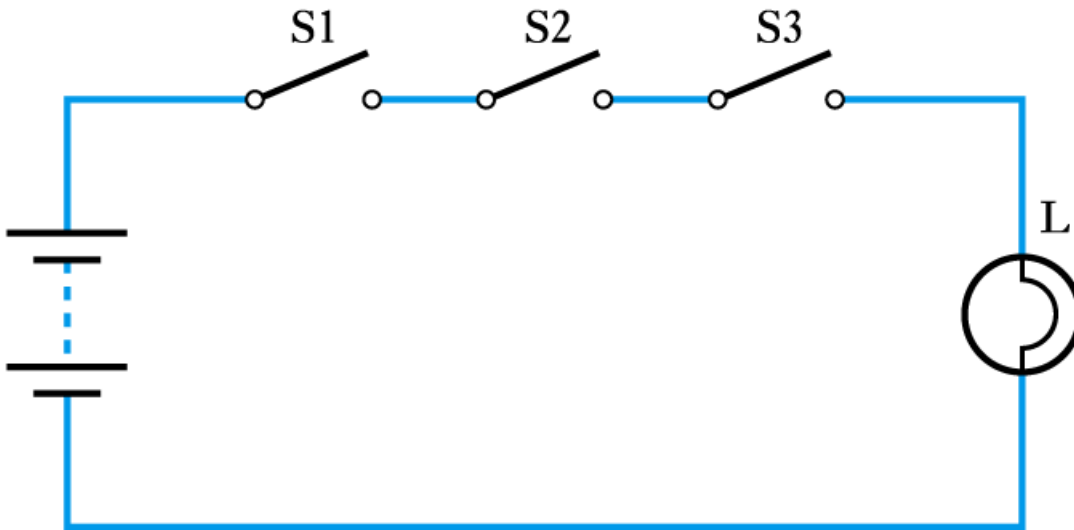


S1	S2	S3	L
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$L = S1 \text{ AND } S2 \text{ AND } S3$$




- Three switches in parallel

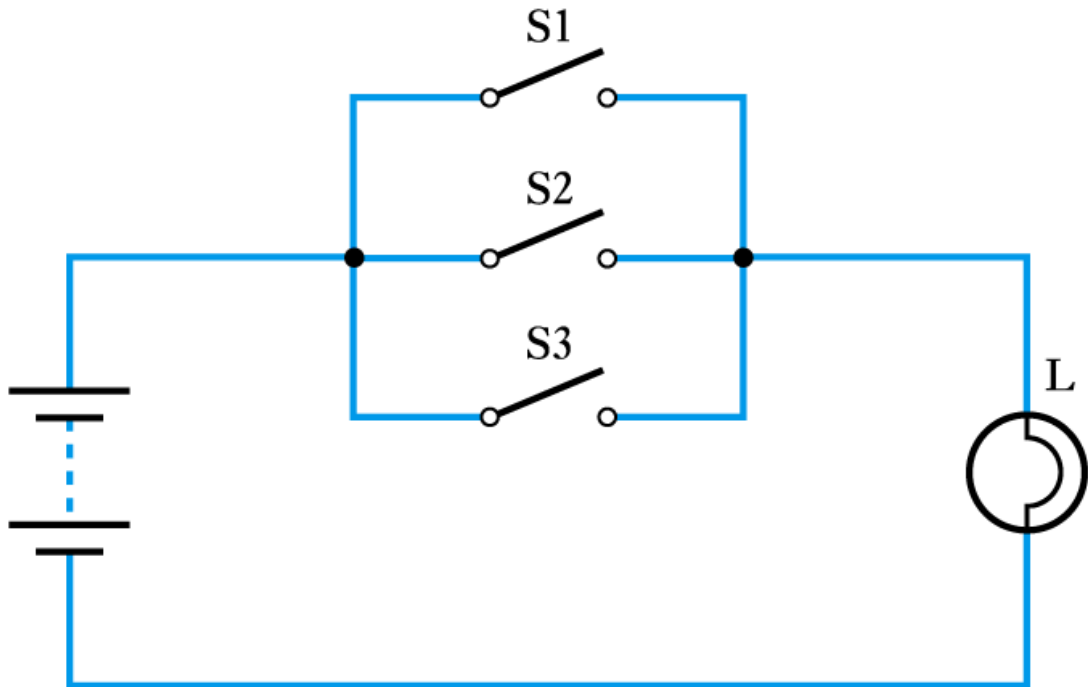

S1	S2	S3	L
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$L = S1 \text{ OR } S2 \text{ OR } S3$$


- A series/parallel arrangement

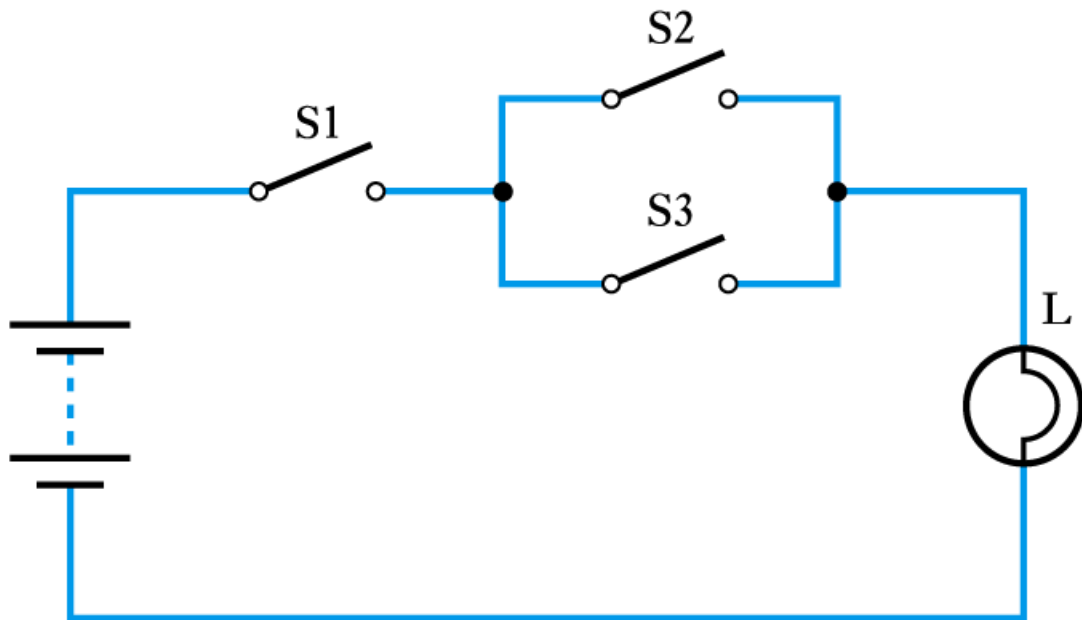

S1	S2	S3	L
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$L = S1 \text{ AND } (S2 \text{ OR } S3)$$

- Representing an unknown network

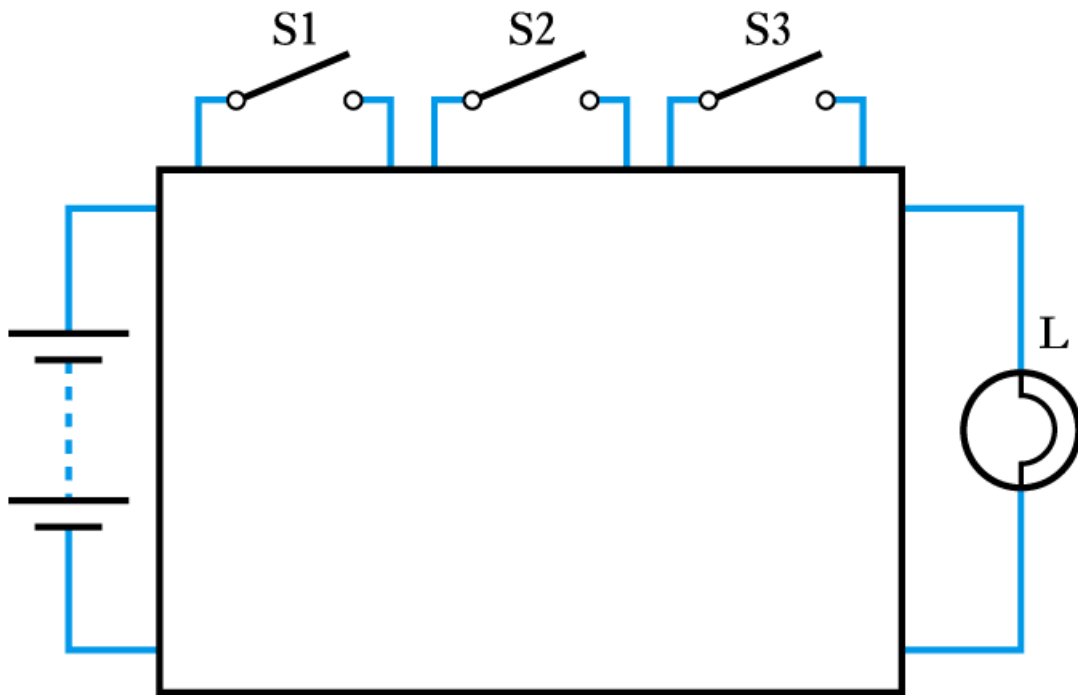

# Logic Gates

- The building blocks used to create digital circuits are **logic gates**
- There are three elementary logic gates and a range of other simple gates
- Each gate has its own **logic symbol** which allows complex functions to be represented by a logic diagram
- The function of each gate can be represented by a **truth table** or using **Boolean notation**

## ■ The AND gate



(a) Circuit symbol

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

(b) Truth table

$$C = A \cdot B$$

(c) Boolean expression

## ■ The OR gate



(a) Circuit symbol


A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

(b) Truth table

$$C = A + B$$

(c) Boolean expression

- The NOT gate (or inverter)

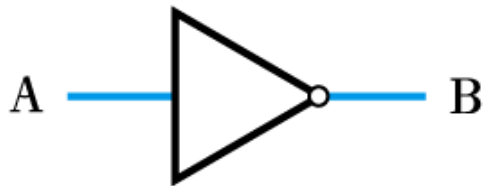

(a) Circuit symbol


A	B
0	1
1	0

(b) Truth table

$$B = \overline{A}$$

(c) Boolean expression

- A logic buffer gate

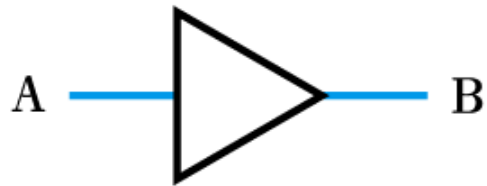

(a) Circuit symbol

A	B
0	0
1	1

(b) Truth table

$$B = A$$

(c) Boolean expression



## ■ The NAND gate



(a) Circuit symbol

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

(b) Truth table

$$C = \overline{A \cdot B}$$

(c) Boolean expression

## ■ The NOR gate



(a) Circuit symbol

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

(b) Truth table

$$C = \overline{A + B}$$

(c) Boolean expression

## ■ The Exclusive OR gate



(a) Circuit symbol

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

(b) Truth table

$$C = A \oplus B$$

(c) Boolean expression

## ■ The Exclusive NOR gate



(a) Circuit symbol

A	B	C
0	0	1
0	1	0
1	0	0
1	1	1

(b) Truth table

$$C = \overline{A \oplus B}$$

(c) Boolean expression

# Boolean Algebra

- **Boolean Constants**

- these are '0' (false) and '1' (true)

- **Boolean Variables**

- variables that can only take the values '0' or '1'

- **Boolean Functions**

- each of the logic functions (such as AND, OR and NOT) are represented by symbols as described above

- **Boolean Theorems**

- a set of **identities** and **laws** – see text for details

## ■ Boolean identities

AND Function	OR Function	NOT function
$0 \bullet 0 = 0$	$0 + 0 = 0$	$\overline{0} = 1$
$0 \bullet 1 = 0$	$0 + 1 = 1$	$\overline{1} = 0$
$1 \bullet 0 = 0$	$1 + 0 = 1$	$\overline{\overline{A}} = A$
$1 \bullet 1 = 1$	$1 + 1 = 1$	
$A \bullet 0 = 0$	$A + 0 = A$	
$0 \bullet A = 0$	$0 + A = A$	
$A \bullet 1 = A$	$A + 1 = 1$	
$1 \bullet A = A$	$1 + A = 1$	
$A \bullet A = A$	$A + A = A$	
$A \bullet \overline{A} = 0$	$A + \overline{A} = 1$	

## ■ Boolean laws


<b>Commutative law</b> $AB = BA$ $A + B = B + A$	<b>Absorption law</b> $A + AB = A$ $A(A + B) = A$
<b>Distributive law</b> $A(B + C) = AB + AC$ $A + BC = (A + B)(A + C)$	<b>De Morgan's law</b> $\overline{A + B} = \overline{A} \cdot \overline{B}$ $\overline{A \cdot B} = \overline{A} + \overline{B}$
<b>Associative law</b> $A(BC) = (AB)C$ $A + (B + C) = (A + B) + C$	<b>Note also</b> $A + \overline{A}B = A + B$ $A(\overline{A} + B) = AB$

# Combinational Logic


- Digital systems may be divided into two broad categories:
  - **combinational logic**
    - where the outputs are determined solely by the current states of the inputs
  - **sequential logic**
    - where the outputs are determined not only by the current inputs but also by the sequence of inputs that led to the current state
- In this lecture we will look at combination logic



## Examples 1,2

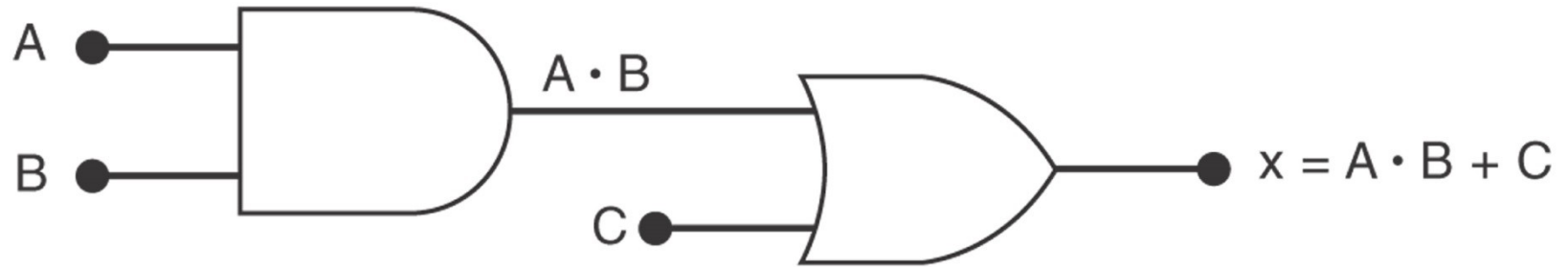


(a)

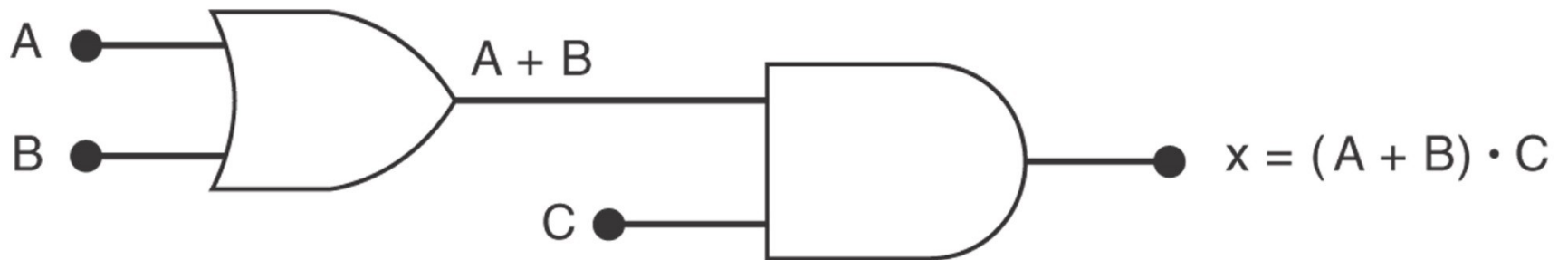


(b)

## Examples 3

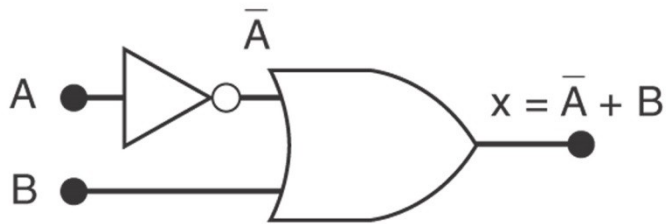


(a)

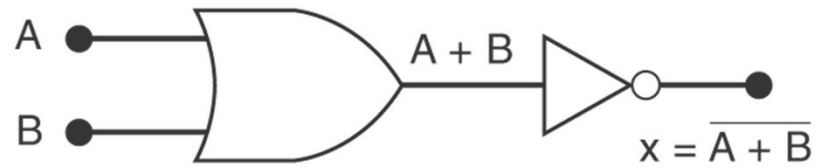


(b)

## Example 4

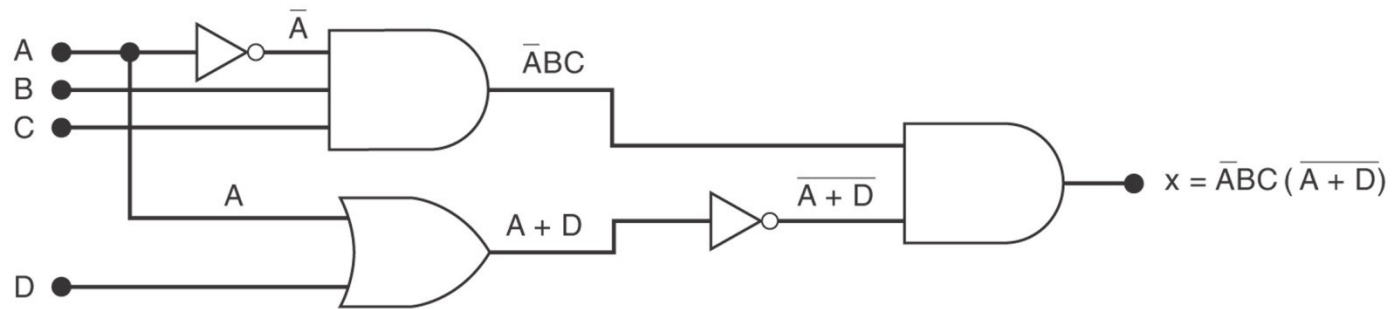


(a)

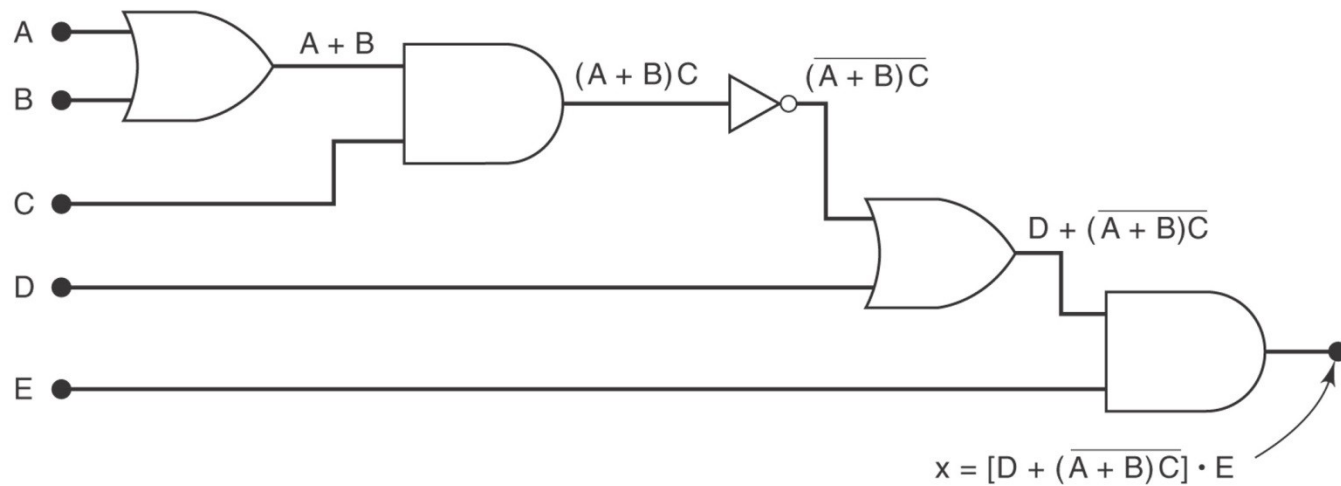

(b)

■ Implementing a function from a Boolean expression  
**Example** –


$$X = A + B\bar{C}$$

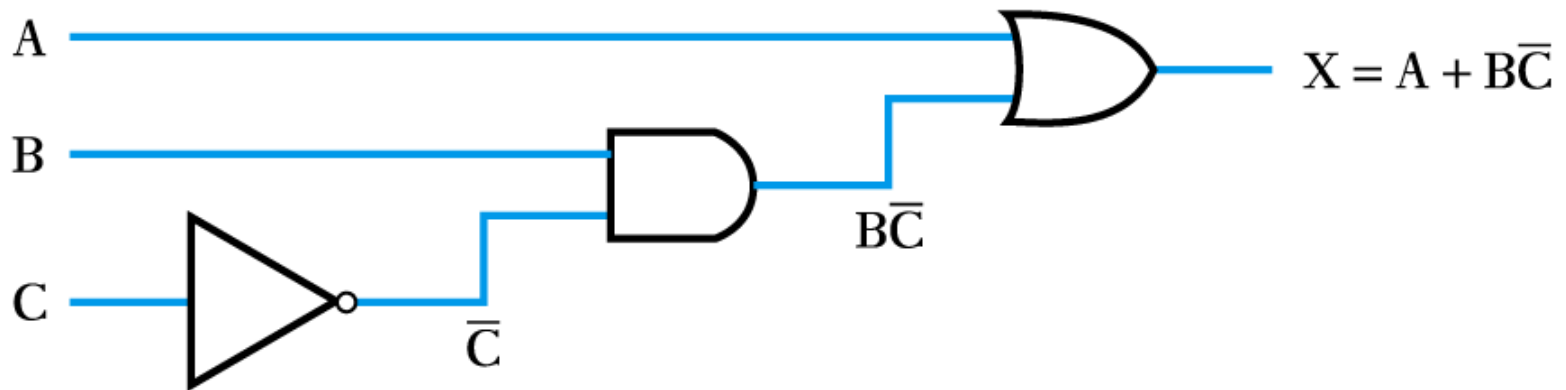

## ■ Implementing a function from a Boolean expression

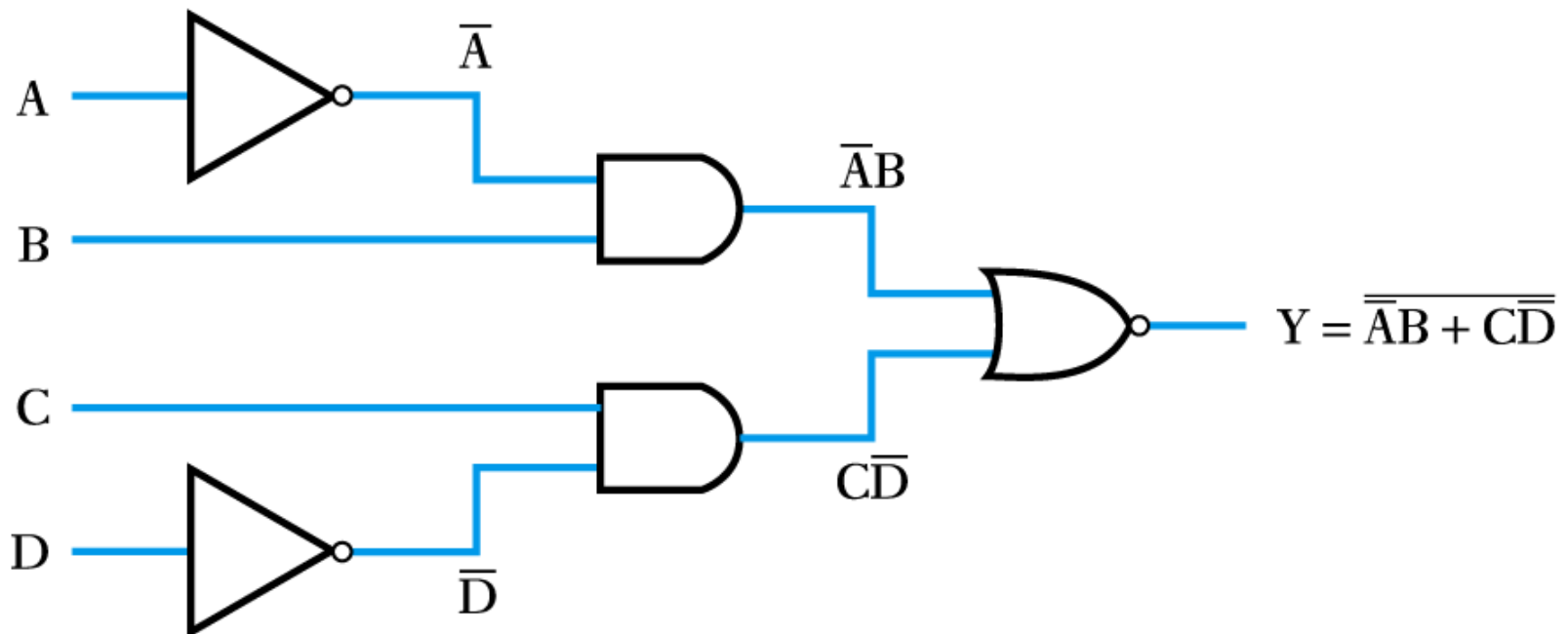
Example –

$$Y = \overline{\overline{A}B + C\overline{D}}$$




- **Generating a Boolean expression from a logic diagram**

**Example –**

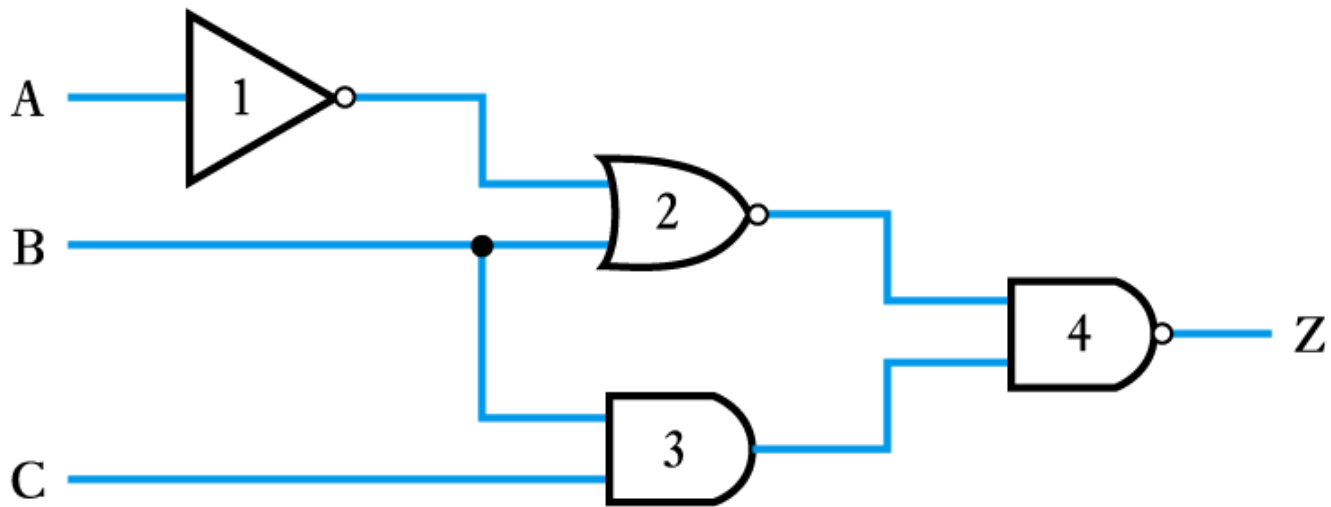
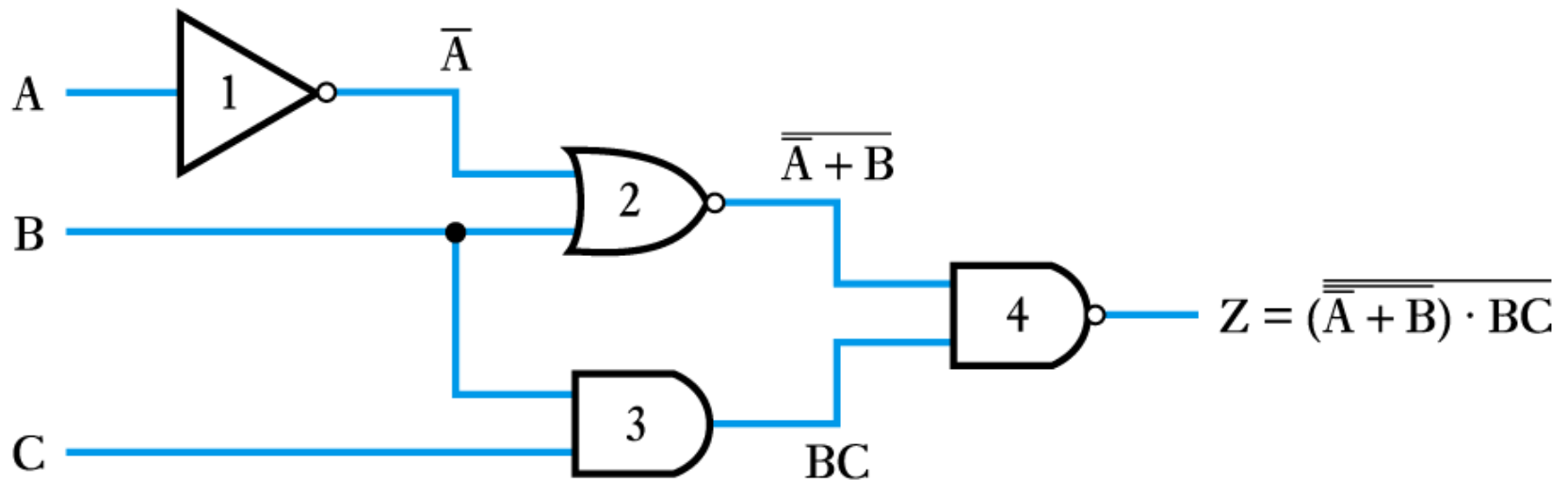
## Example (continued)

- work progressively from the inputs to the output adding logic expressions to the output of each gate in turn



## ■ Implementing a logic function from a description

### Example –

The operation of the Exclusive OR gate can be stated as:

*“The output should be true if either of its inputs are true, but not if both inputs are true.”*

This can be rephrased as:

*“The output is true if A OR B is true, AND if A AND B are NOT true.”*

We can write this in Boolean notation as

$$X = (A + B) \cdot \overline{(AB)}$$




## Example (continued)

The logic function

$$X = (A + B) \cdot (\overline{AB})$$

can then be implemented as before

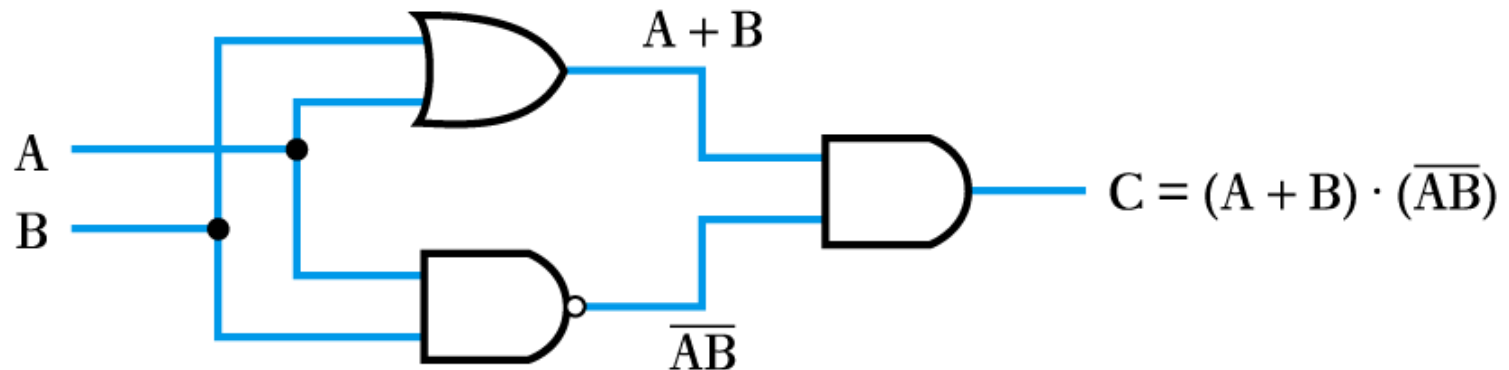

## ■ Implementing a logic function from a truth table

### Example –

Implement the function of the following truth table


A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

- first write down a Boolean expression for the output
- then implement as before
- in this case

$$X = \bar{A} \bar{B} C + A \bar{B} C + A B \bar{C}$$
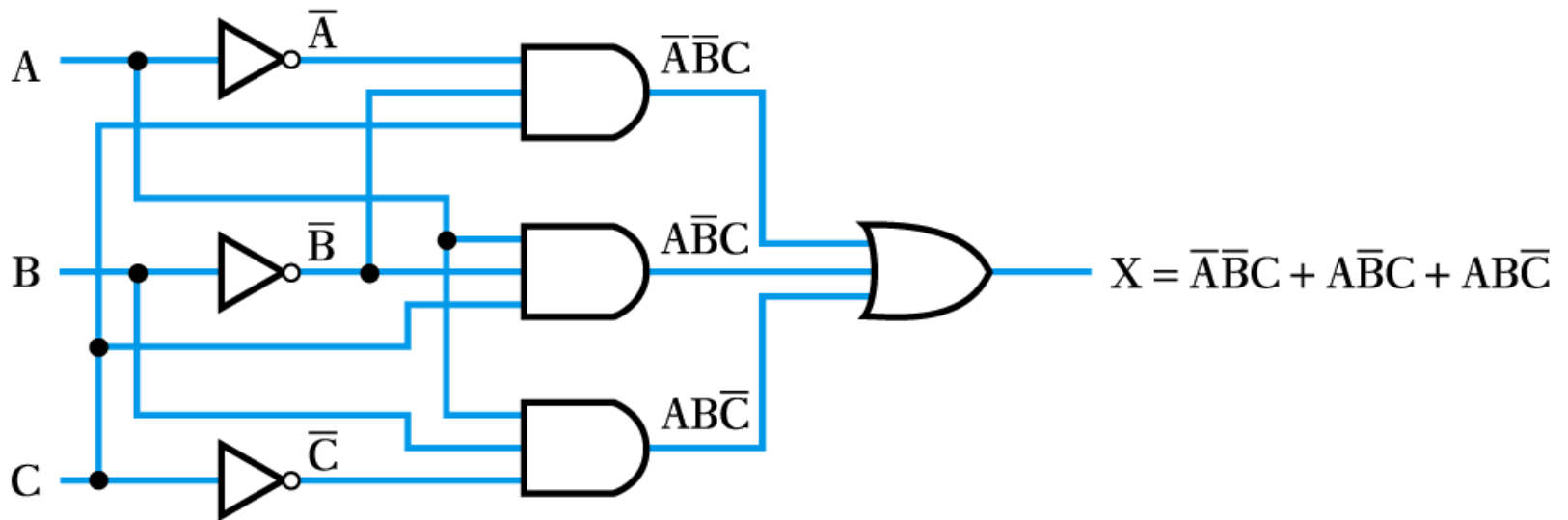
## Example (continued)

The logic function  $X = \bar{A} \bar{B} C + A \bar{B} C + A B \bar{C}$  can then be implemented as before



- In some cases it is possible to *simplify* logic expressions using the rules of Boolean algebra

**Example –**

$X = ABC + \bar{A}BC + AC + A\bar{C}$  can be simplified to  $X = BC + A$   
hence the following circuits are equivalent

