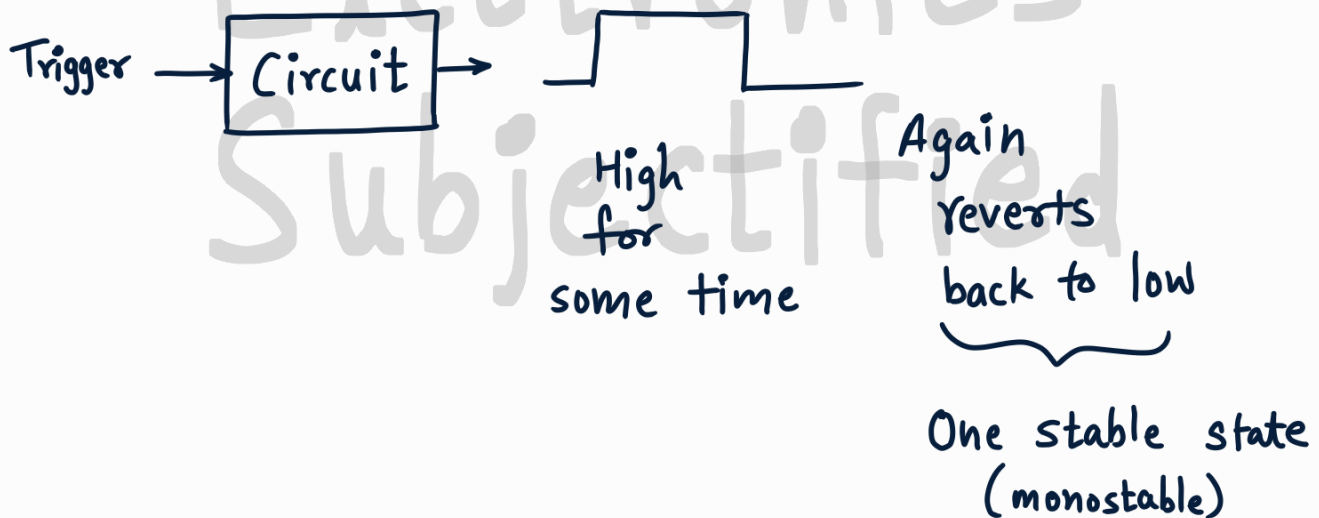



Monostable Multivibrator Using 555

↳ one shot multivibrator



Needs external trigger pulse for output = 1 (High)



Circuit Diagram

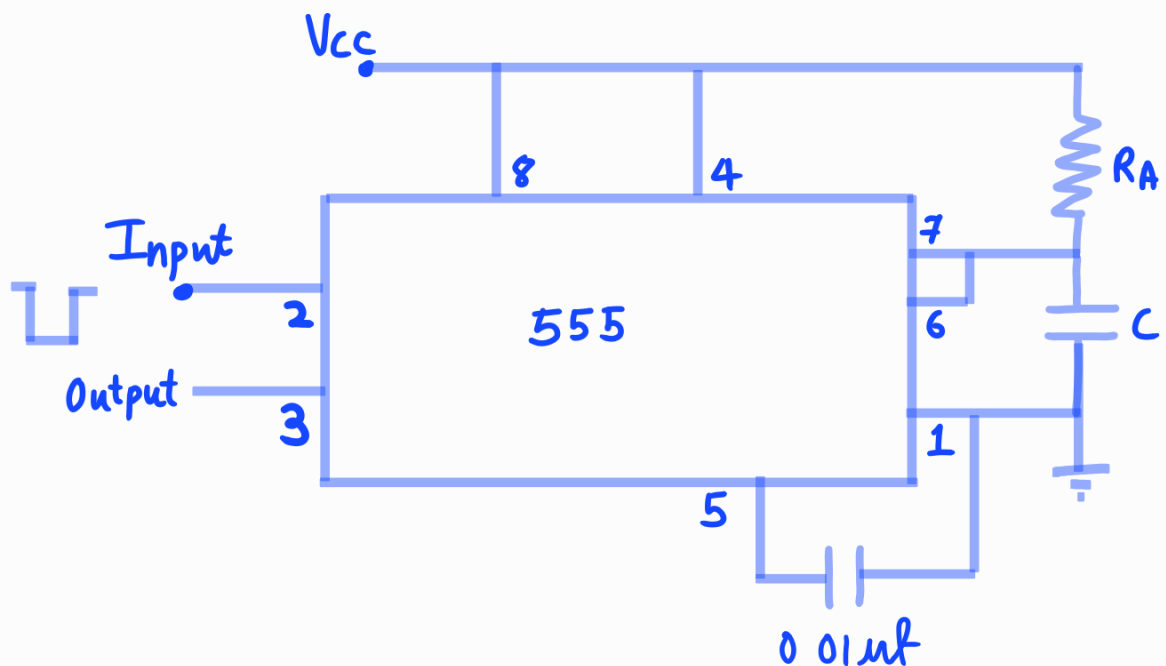

Waveforms

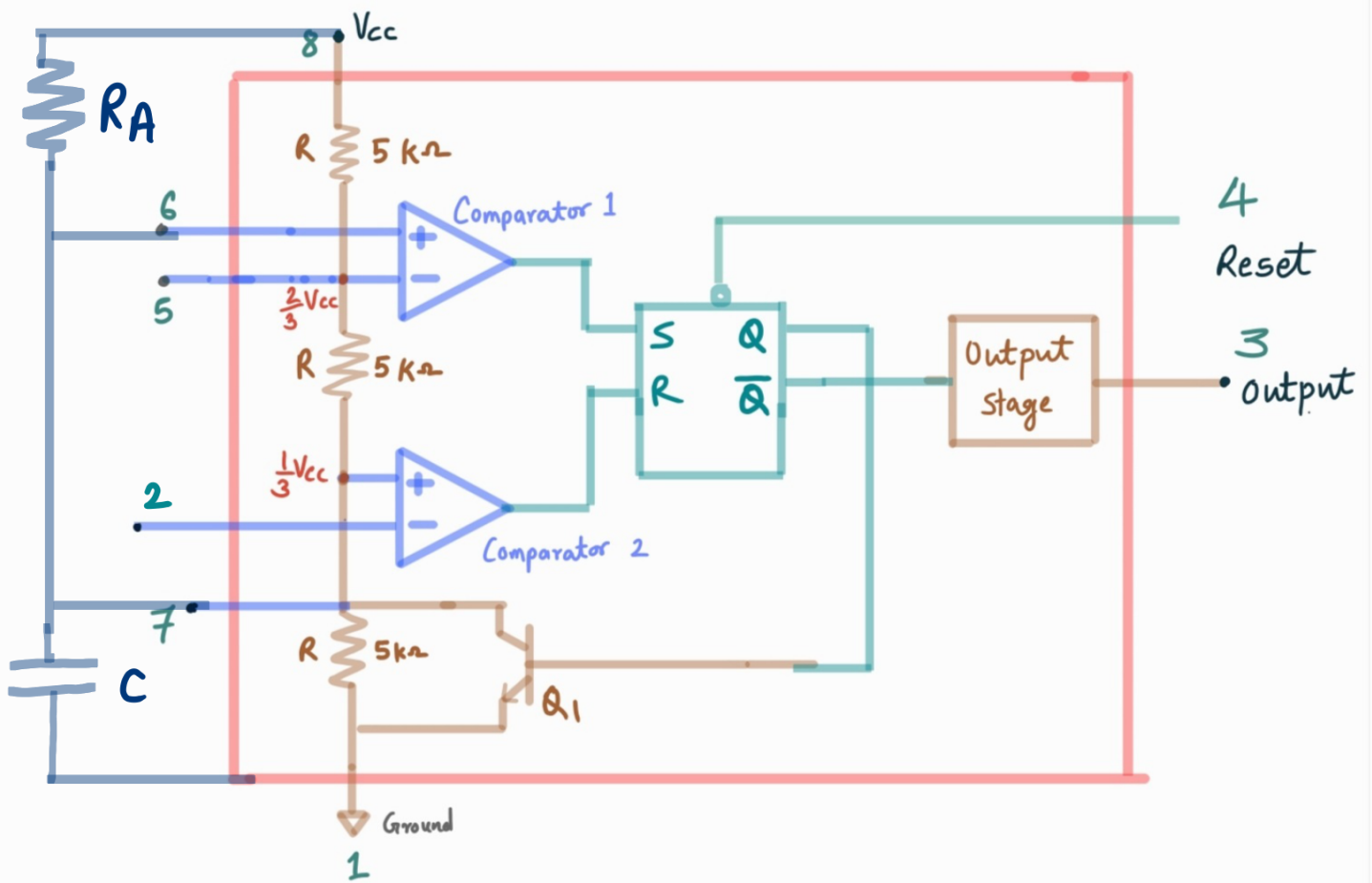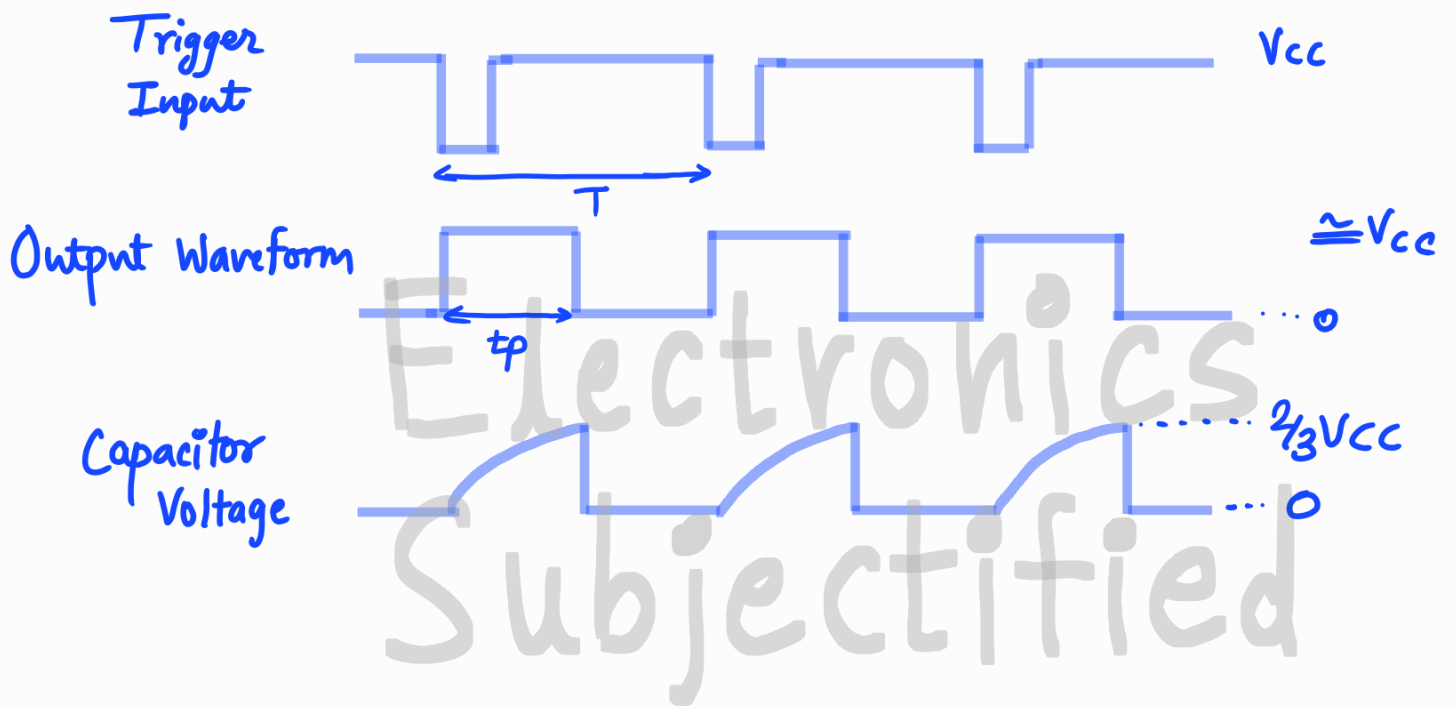

Working

- Initially when the circuit is in stable state

O/p is low \rightarrow Transistor is on

Capacitor is shorted out to ground

- After negative trigger pulse to pin 2

$V_{tr} < \frac{1}{3} V_{cc} \rightarrow$ O/p of comparator 2 = High

- Transistor off \rightarrow Open Circuit

FF reset $Q=0, \bar{Q}=1$

Capacitor C starts charging towards V_{cc}
through R_A

- when $V_C = \frac{2}{3} V_{cc}$

$V_C > \frac{2}{3} V_{cc} \rightarrow$ O/p of comparator 1 = High

O/p of circuit = Low (\bar{Q})

FF set $Q=1, \bar{Q}=0$

Transistor is ON \rightarrow C discharges through R_A

Output of circuit remains low

till the trigger is applied again

Output remains HIGH for

$$t_p = 1.1 R A C \quad \text{seconds}$$

Short Working

